

# Lecture 10: Gate Delay and Power

---

Matthew Guthaus

Professor

UCSC, Computer Science & Engineering

<http://vlsida.soe.ucsc.edu>

mrg@ucsc.edu




# Today's Topics

---


- Switched transistor networks
- First-order gate delay model
  - Elmore Delay
- Power consumption




# Switch Model... Again

 


# Transistor W and L

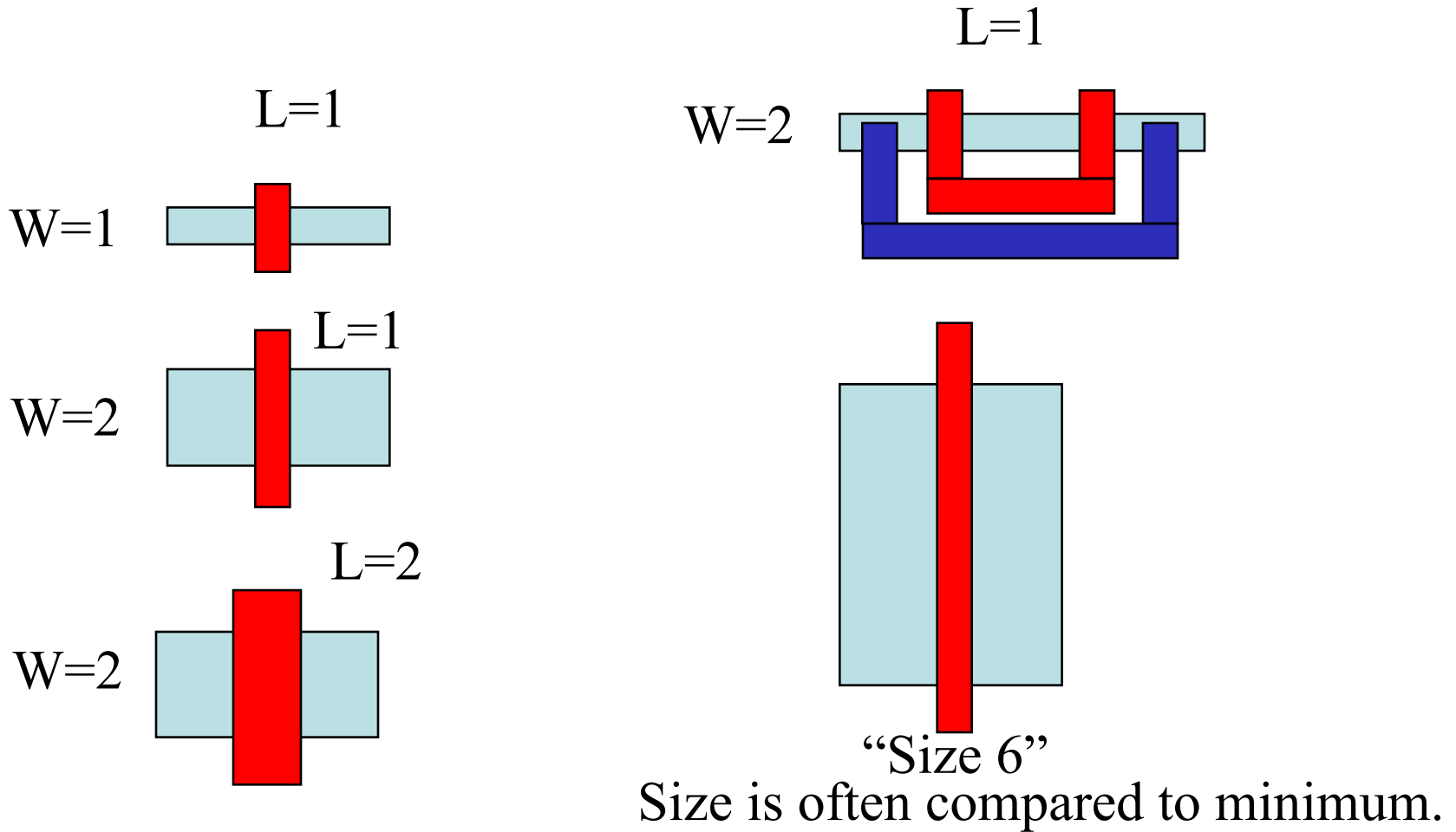

# Transistor as a Switch... Again

 

Resistors should be linear,  
right?

 

$$R = V_{ds} / I_d$$

$$R_{on} \cong \text{average}(R_0, R_{mid})$$

$$R_{eq} \propto L/W$$

# Req, W, and L

---

Resistance goes up as L goes up

“Resistance in series”

Resistance goes down as W goes up

“Resistance in parallel”

Req is proportional to L/W


Each transistor will have a W and L, if L is not given, it is minimum.

$$\text{Req} \propto L/W$$




# PMOS vs NMOS Resistance

Vary “ratio” of PMOS to NMOS width

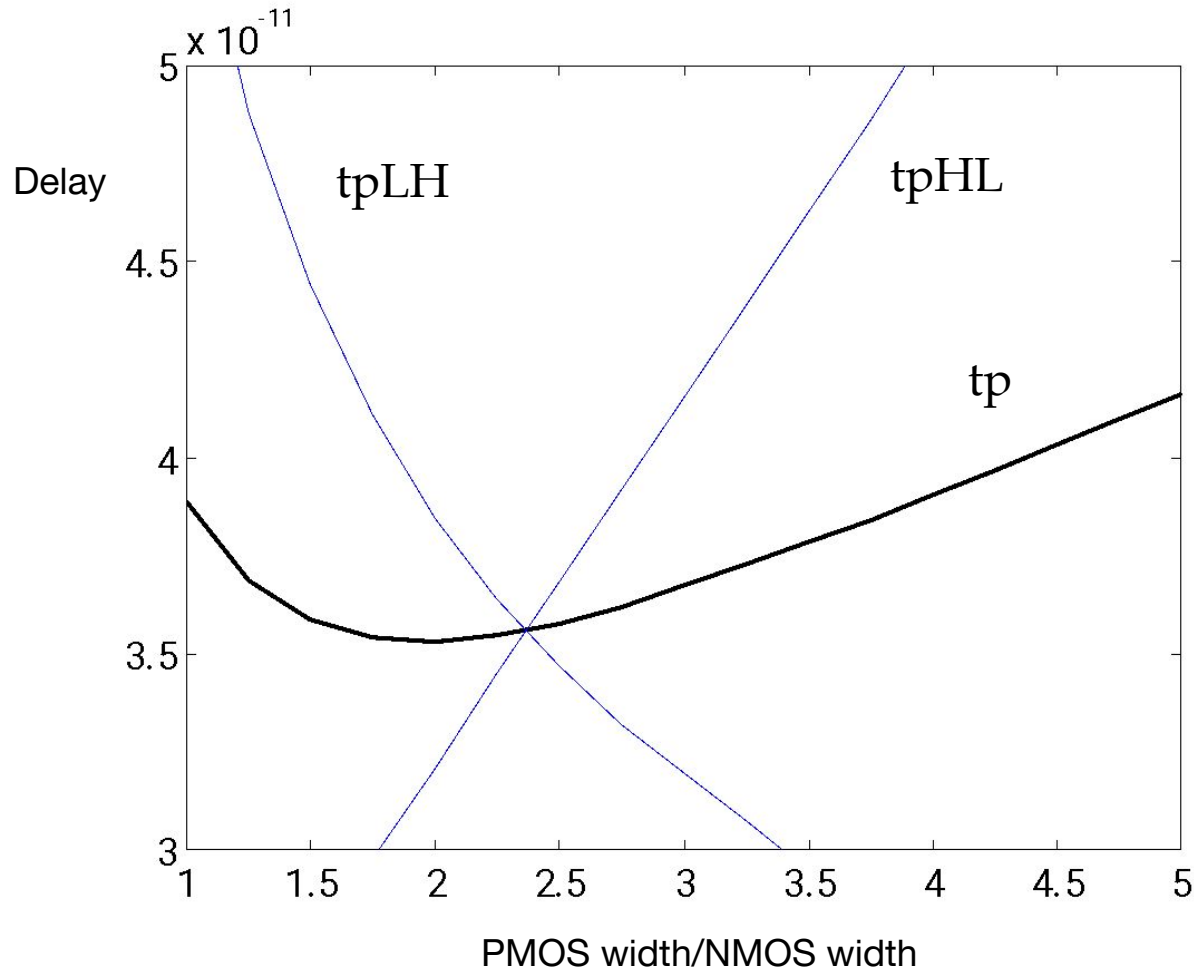

$$\beta = W_p / W_n$$

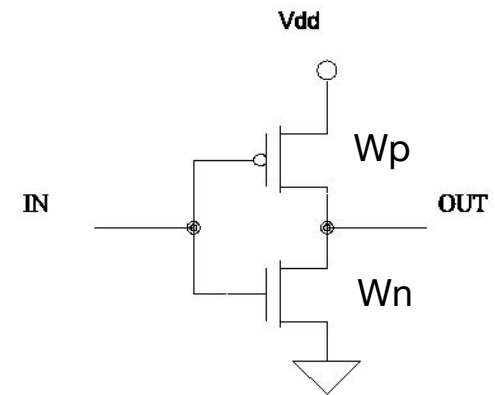



# Relative resistances

- We often don't need  $R$  explicitly, but instead know that:
  - $2W$  has half the  $R$  of  $W$
  - $4W$  has  $\frac{1}{4}$  the  $R$  of  $W$
  - etc.
- Device types
  - PMOS is twice the  $R$  of same size NMOS
  - PMOS of size  $2W$  is same  $R$  as NMOS of size  $W$






# First Order (Static) Analysis

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

# Delay vs Rise/Fall Definitions

 

 
# Switch Model

Which is faster? (Assume same size transistors)



$$1/R_{eq} = 1/R_a + 1/R_b$$


*Sometimes* double current

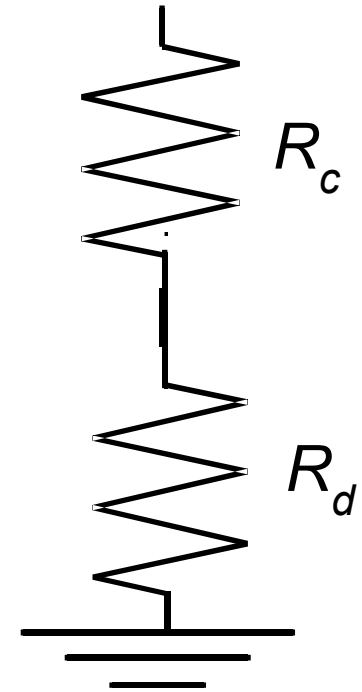


$$R_{eq} = R_a + R_b$$

Half the current

# Transient (Elmore) Delay

 
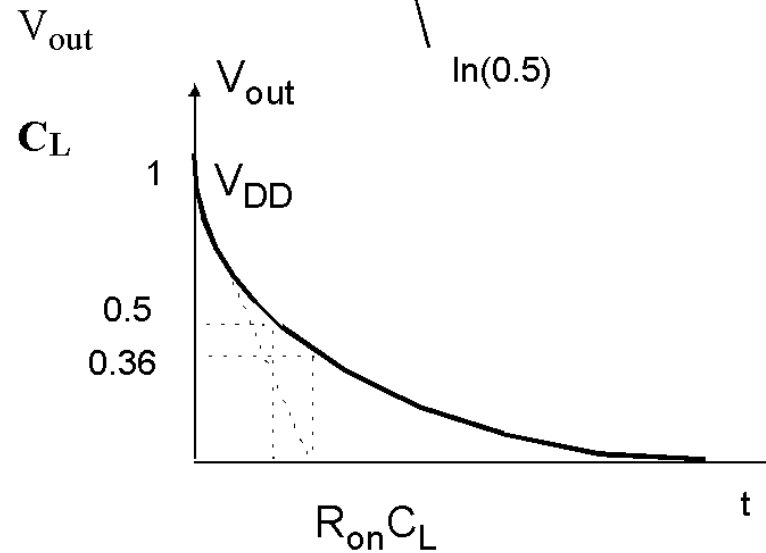
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$



# Intuition Check

---

$$\text{Delay} = 0.69RC$$

What happens if you drive twice the fanout?

What happens if you use a “2x” gate instead of a “1x” (this is drive strength)?



# Pros/Cons of Elmore Delay



---

- Cons
  - Input is an ideal step
  - Assumes resistor model
  - Ignores short-circuit current
  - Output capacitance computation
    - Summing all the fanout and wires is pessimistic
    - Most tools use “effective capacitance”
- Pros
  - Simple and intuitive
  - Fast
  - Good fidelity, but not accuracy



# PMOS vs NMOS Resistance




Vary “ratio” of PMOS to NMOS width

  

# Scaling of NAND Delay

Series transistors in pull down add up resistance.


More series resistance means more delay.

   





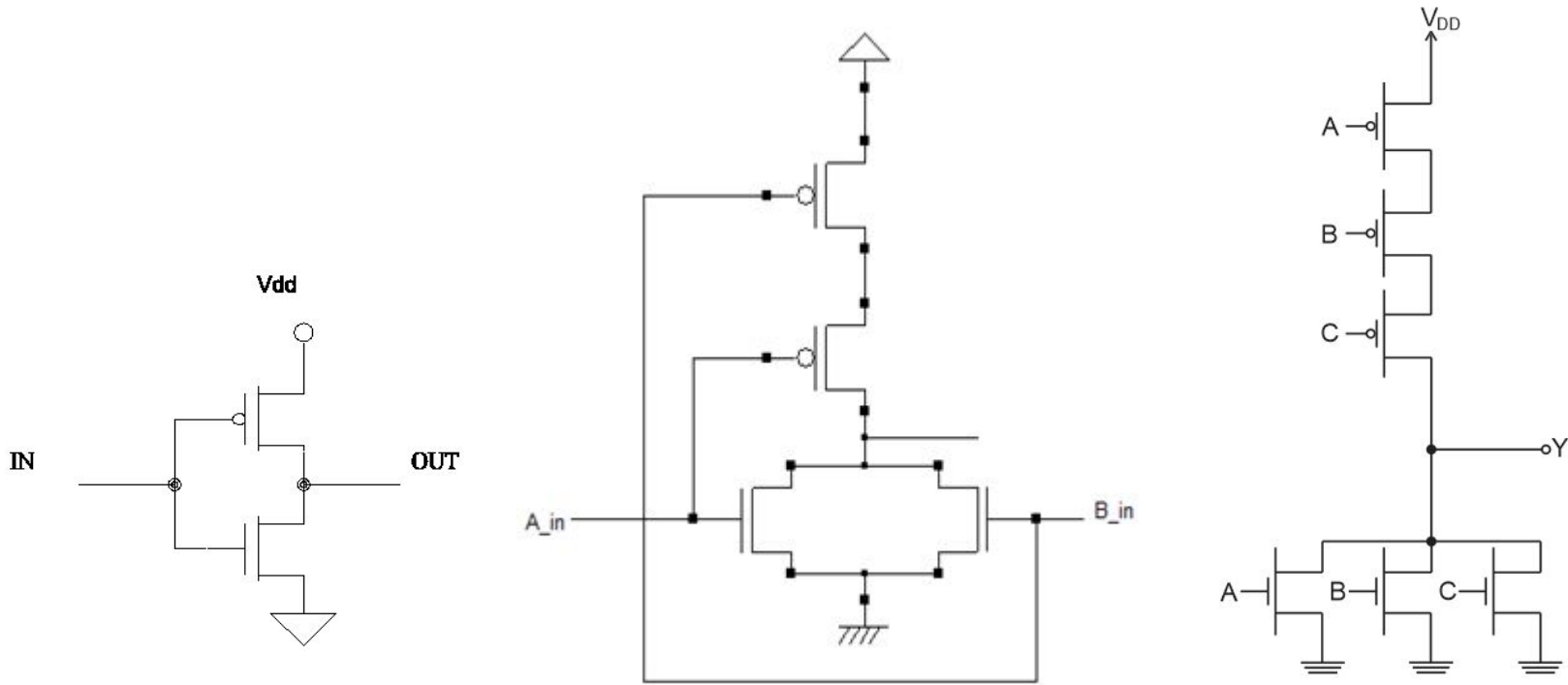
# Scaling of NOR Delay

Similar to NAND, but pull up delay increases.





# Equivalent Width Gates

   

$R_{eq} \propto L/W$





# NAND3 and NAND4

  

 
 
# Diffusion Capacitance

Diffusion capacitance proportional to transistor width

Capacitance related to perimeter and area




# Visualizing the Capacitances


 
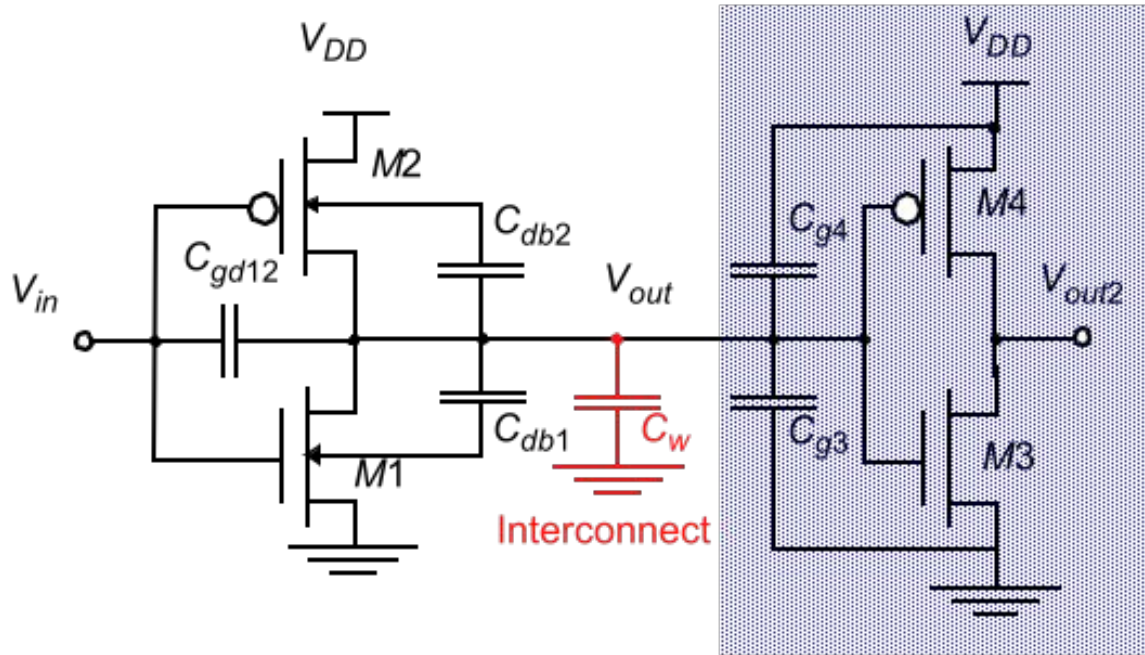


Fanout



Simplified Model

 

# How much self-loading capacitance?

 
 
 


# How much self-loading capacitance?

  
   
# Sizing of Gates


- Relative sizes are preserved
- inv\_1, inv\_2, inv\_4 means  $S=1$ ,  $S=2$ ,  $S=4$




 
# Self Loading

Consider a gate driving a fixed output cap.



# Where does power go in CMOS?

---

- **Dynamic Power Consumption**

Charging and Discharging Capacitors

- **Short Circuit Currents**


Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors



# Power: Dynamic


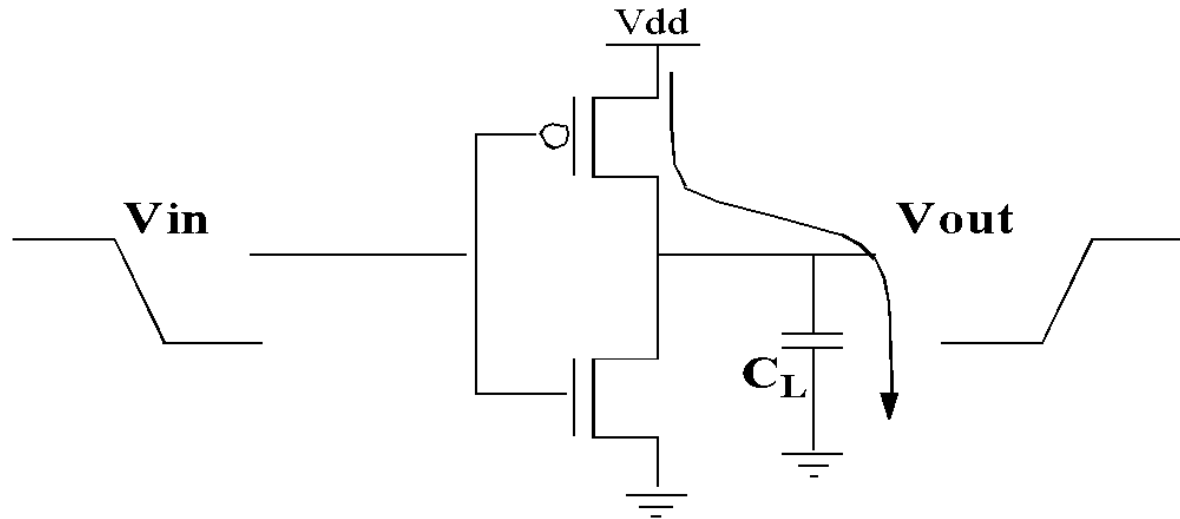


$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- **Not a function of transistor sizes!**
- **Need to reduce  $C_L$ ,  $V_{dd}$ , and  $f$  to reduce power.**


# Power: Leakage

 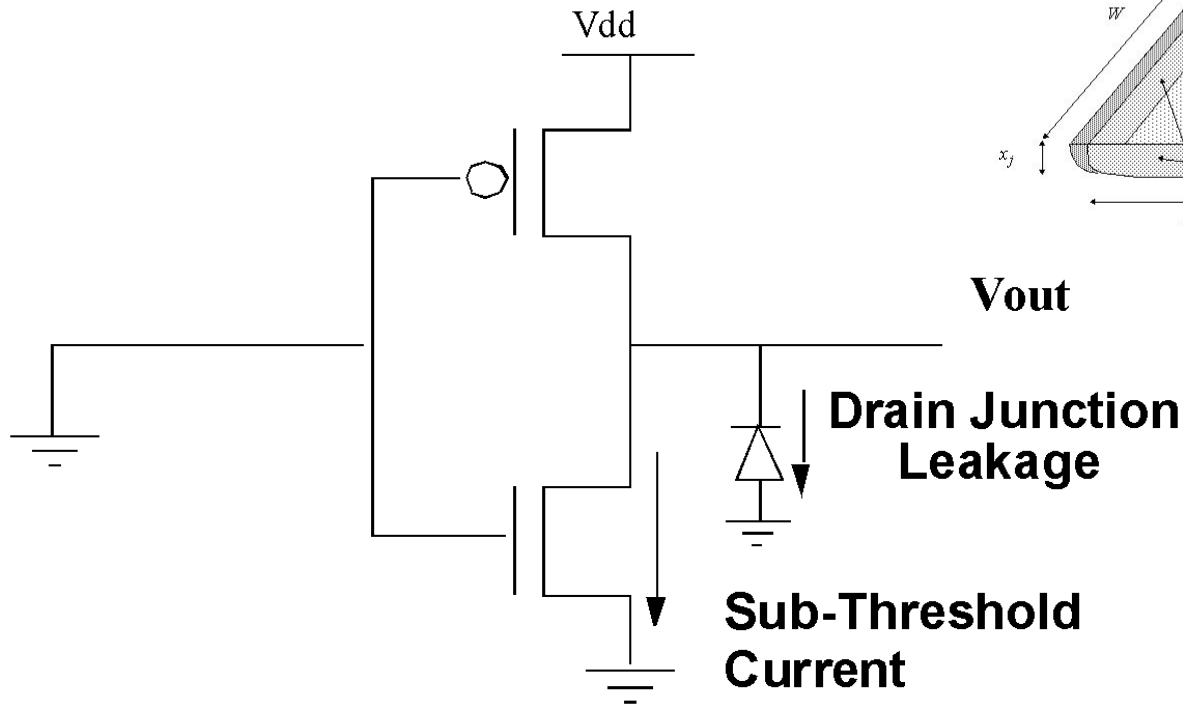


**Sub-Threshold Current Dominant Factor**
 
# Power: Short Circuit

Both PMOS and NMOS are “on” while a signal is transitioning



Large capacitive load

 

Small capacitive load

# (Some) Low Power Techniques

---

- Reduce capacitance
  - Use smaller size gates
  - Shorten wires
- Reduce switching
  - Lower frequency
  - Logic gating
- Lower vdd
- Increase  $V_{th}$  (lowers leakage)



# Power Reports

OpenLane/designs/picorv32a/runs/CLASS/reports/signoff/31-rcx\_sta.power.rpt

```
report_power
```

===== Typical Corner =====

Group	Internal Power	Switching Power	Leakage Power	Total Power (Watts)	
Sequential	3.96e-03	1.51e-03	1.35e-08	5.48e-03	25.5%
Combinational	6.79e-03	9.23e-03	5.99e-08	1.60e-02	74.5%
Macro	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Pad	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.0%
Total	1.08e-02	1.07e-02	7.33e-08	2.15e-02	100.0%
	50.0%	50.0%	0.0%		



# Next Lecture

---

- Interconnect

